DN06004/D



Design Note - DN06004/D

SEPIC LED Driver

ON Semiconductor

Device	Application	Input Voltage	Output Power	Topology	I/O Isolation
CS5171	Miners Light	4 Vdc	2 W	SEPIC	NO

Other Specifications							
	Output 1	Output 2	Output 3	Output 4			
Output Voltage	3.5 V	N/A	N/A	N/A			
Nominal Current	350 mA	N/A	N/A	N/A			


Minimum Efficiency	70%		
Operating Temp. Range	0 to +70°C		

Circuit Description

This application is for the LED driver to be powered from a source that can be higher or lower than the LED voltage and must be efficient as possible. The SEPIC topology was chosen. The schematic in the following page shows a 4 V SEPIC LED driver using the CS5171 as a DC-DC boost regulator. The CS5171 operates at 260 KHz with about 65% efficiency with a 4.0V input. The MBRM110LT1 is a 10V schottky diode with a forward drop of < 0.3V. The NCS2001 operates as amplifier for the current sense voltage across R2 and drives the feedback pin on the CS5171.


Key Features


- SEPIC LED Driver
- 350 mA LED Current

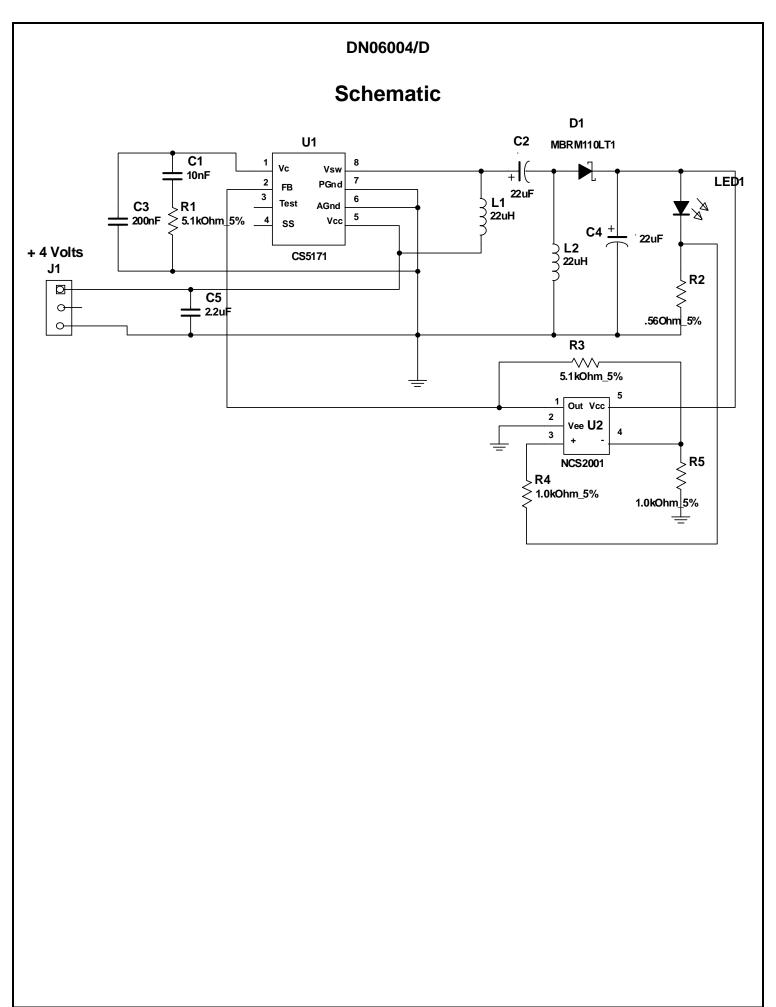




Layout

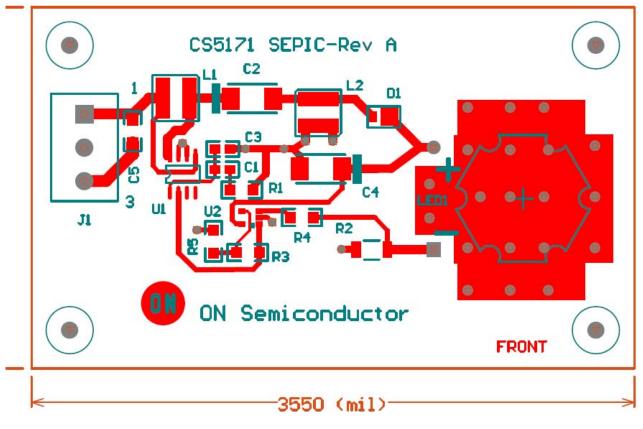

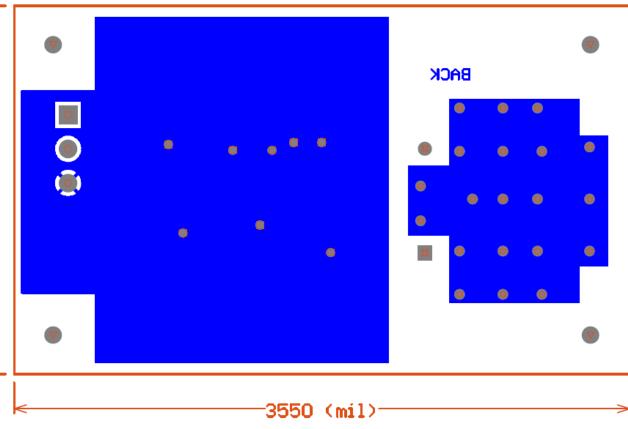

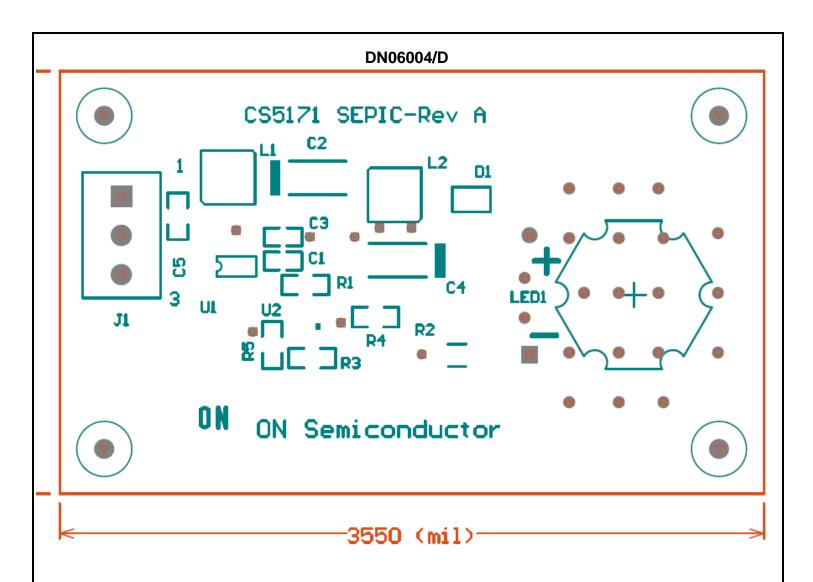

DN06004/D

Bill of Materials

Ref.	Qty.	Description	Value	Package	Vendor	Vendor PN	Digikey #
U1	1	IC Boost Controller		SO-8	ON Semi	CS5171ED8	
U2	1	Amplifier		SOT23-5	ON Semi	NCS2001SN2T1	
D1	1	Diode	10 V Schottky	Powermite	ON Semi	MBRM110LT1	
LED1	1			STAR / O	LUXON	LXHL-NW98	
J1	1				Phoenix Contact	1715035	
C1	1	Capacitor	.01 uf	805	Panasonic	ECJ-2VB1H103K	PCC103BNCT-ND
C2	1	Capacitor	22 uf	smd	Panasonic	EEF-CD1B220R	PCE3168CT-ND
C3	1	Capacitor	200 nf	805	Panasonic	ECJ-2VB1C224K	PCC1816CT-ND
C4	1	Capacitor	22 uf	smd	Panasonic	EEF-CD1B220R	PCE3168CT-ND
C5	1	Capacitor	2.2 uf	1206	Panasonic	ECJ-3YB1C225K	PCC1931TR-ND
R1	1	Resistor	5.1 K ohm	1206	Panasonic		P5.1KECT-ND
R2	1	Resistor	.56 ohm 1%	1206	Panasonic		P.56RCT-ND
R3	1	Resistor	5.1 K ohm 1%	1206	Panasonic		P5.1KFCT-ND
R4	1	Resistor	1 K ohm 1%	1206	Panasonic		P1.0KFCT-ND
R5	1	Resistor	1 K ohm 1%	1206	Panasonic		P1.0KFCT-ND
L1	1	Inductor	22 uh	smd	Coil_craft	MSS6132-223MXD	
L2	1	Inductor	22 uh	smd	Coil_craft	MSS6132-223MXD	
DCD	1	COE474 OFDIC wassing a series				CC5474 Day A	
PCB	1	CS5171 SEPIC raw board				CS5171 Rev A	

© 2006 ON Semiconductor.

Disclaimer: ON Semiconductor is providing this design note "AS IS" and does not assume any liability arising from its use; nor does ON Semiconductor convey any license to its or any third party's intellectual property rights. This document is provided only to assist customers in evaluation of the referenced circuit implementation and the recipient assumes all liability and risk associated with its use, including, but not limited to, compliance with all regulatory standards. ON Semiconductor may change any of its products at any time, without notice.

Design note created by Roger Miller, e-mail: roger.miller@onsemi.com